

# M152A Lab 3: Stopwatch

Ryan Stenberg      Rodrigo Valle

February 28, 2017

## Introduction

The stopwatch we designed has a basic clock that has two two-digit fields: minutes and seconds, which are displayed on a four digit seven segment display. Additional features of the stopwatch include:

- **Adjust Mode:** entered when switch zero is flipped. In adjust mode, the currently selected field will visibly blink as the numbers in that field begin increasing at 2Hz. All other fields of the stopwatch will not be updated in adjust mode.
- **Select:** switch one allows a user to select which field they wish to adjust in adjust mode.
- **Reset:** when the reset button is pressed, the clock will begin counting from zero.
- **Pause:** when the pause button is pressed, it toggles the stopwatch's pause mode. In pause mode, the stopwatch's clock will stop counting seconds.

## Design

To make this project easier to work with and split up tasks, we relied very heavily on reliable independent modules that were tested individually and designed to perform only one action (where feasible) – and do it well.

## Modules

Our design was modularized into the following components:

- **clock\_div:** a clock divider that accepted the 200 MHz FPGA master clock as input and divided it into a 1 Hz clock for the stopwatch to count seconds, a 2 Hz clock which was used for the “fast increment” during adjustment mode, a 4 Hz clock which was used for the display blinking,

and a 400 Hz clock which was used to multiplex digits across each of the 4 seven segment displays.

- **dec\_counter**: a clocked counter that simply counts to ten and supports reset. The `c_out` output will be set high when the counter overflows.
- **counter**: created using two `dec_counters`, this counter represents a field on our stopwatch clock (e.g. the minutes or seconds field).
  - inputs: takes a clock input which decides how fast to count, and a reset input which will cause the counter to begin counting from zero.
  - outputs: a tens place count and a ones place count which together represent a number. Also outputs a `c_out`, which will be set high whenever the counter overflows, allowing us to chain these counters.
- **debouncer**: a simple state machine to detect the falling edge of a noisy signal. It takes a button as input and waits until it registers a steady state followed by a drop off, and then synchronizes the debounced output on a clock edge.
- **ssd\_converter**: a simple combinational logic circuit which accepts a number as input and outputs the correct segments to light up on the seven segment display.
- **blink**: this module sits between `ssd_converter` and `ssd_driver` and blinks input digits from `ssd_converter` on and off with the frequency of a given clock if the enable input is set high. Digits will not blink and simply pass through the module if the enable input is low.
- **ssd\_driver**: this module is responsible for multiplexing four seven segment display input signals across the 4 seven segment displays. This is done by rotating which anode is currently active among the four anodes, and piping in the corresponding cathodes for that anode.
- **stopwatch**: the top level module which glues together the other modules we've specified here. It handles taking input from the physical FPGA controls and giving this input to submodules that need it (along with some control logic).

## Module Schematic

We've labeled the components on this schematic to give a better sense of how these modules fit together:

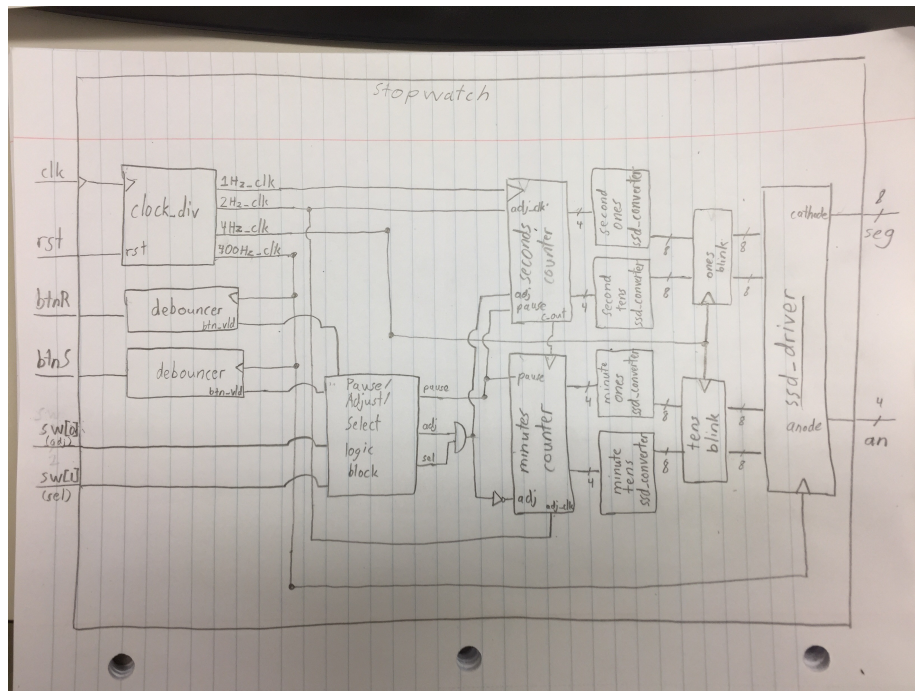


Figure 1: This schematic details the inputs and outputs of our stopwatch along with how it interacts with the other modules that its composed of.

## Debouncer State Machine

We used this state machine diagram to implement our debouncer; with a relatively low sample rate, checking for two bits in a row followed by a zero was more than enough to allow for responsive buttons without noise.

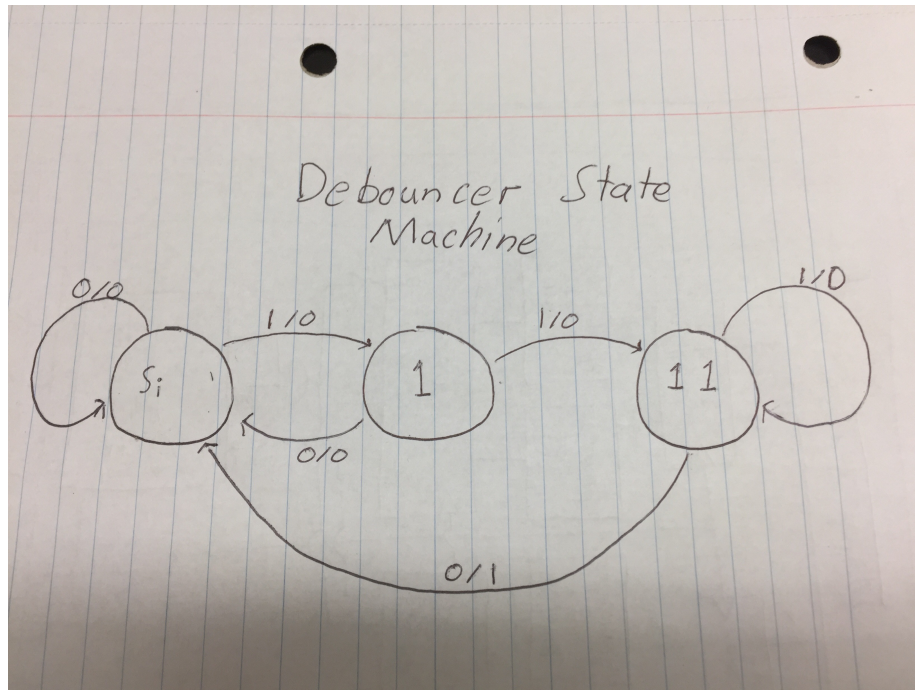


Figure 2: This state machine diagram models the state logic that our debouncer module depends on.

## Bugs

- **blink.v:** Blink logic was originally in `ssd_converter` module. This made it difficult to blink on and off at 4Hz while updating the seven segment display at 400Hz. As a result, our seven segment display wasn't blinking in adjust mode. Eventually we separated it out into its own module called `blink.v` which was placed as an intermediary between `ssd_converter` and `ssd_driver`. This allowed us to tell the `ssd_driver` to show nothing every 4Hz.
- **counter.v:** Had an off by one error that caused our seconds and minutes to reset at 50 instead of 60. This was simply a comparison error in which we reset the tens spot once a positive clock edge hit and the tens digit became 5. This was fixed by changing this comparison to wait for 59 seconds/minutes before resetting to 0.
- **ssd\_converter.v:** Was converting all 6s to 5s so that our seven segment display counted up with the following sequence ...3,4,5,5,7,8... The bug was in the switch statement where we had accidentally routed binary 6 to the cathode display of 5. This was also a quick fix once we isolated this problem.
- **Reset:** Pressing reset wouldn't reset the tens in minutes or seconds (the ones would get reset). This bug was in the `counter.v` module. We were only resetting the tens digit if the reset was being held down while the ones digit incremented from 9  $\rightarrow$  10 (overflow). Of course this never occurred because when the reset button was pressed, the ones digit was set to 0 and could not increment. This was fixed by changing our if-else statements to allow reset to reset both the ones and tens digits with the next clock cycle.

## Simulation Documentation

We tested all basic functionality of a stopwatch including counting up, reset, pause, adjust, and select (seconds & minutes). In doing so we kept an eye out for the following events and edge cases:

- adjust mode caused whichever set of digits (seconds/minutes) was selected to blink and increase at an elevated speed
- pause stopped the stopwatch from all increments until toggled back off
- the seven segment display showed all 10 possible digits correctly (0-9)
- the seven segment display rotated anodes fast enough to not be noticeable to the human eye
- incrementing from 59 seconds to 1 minute and also 59 minutes back to 0 minutes

We created testbenches for several individual modules. These test benches, along with the waveforms they produced are provided below.

counter\_\_tb.v

 


Figure 3: The resulting waveform after running our counter testbench.

This testbench exercises the counter module through all possible states by clocking it and waiting long enough for the counter to overflow. Any errors in output will be noticed visually as counter outputs are printed to the screen.

```
module counter_tb;
    reg clk, rst;
    wire [3:0] count_ones;
    wire [3:0] count_tens;
    wire c_out;

    initial begin
        clk = 0;
        rst = 0;
        #50 $finish;
    end

    always begin
        #0.5 clk = ~clk;
    end

    always @(posedge clk) begin
        $display("count: %d%d\n", count_tens, count_ones,
                "c_out: %b\n", c_out);
    end

    counter counter_inst(
        .clk(clk),
        .rst(rst),
        .count_ones(count_ones),
        .count_tens(count_tens),
        .c_out(c_out)
    );
endmodule
```

## dec\_counter\_tb.v



Figure 4: The resulting waveform after running our dec\_counter testbench.

This testbench exercises the dec\_counter module until it overflows, printing out the count and c\_out of the dec\_counter to the screen as it counts. Any errors will be inspected visually on the screen. This module is very simple, so this testbench is more of a sanity check for us.

```
module dec_counter_tb;
    reg clk, rst;
    wire c_out;
    wire [3:0] count;

    initial begin
        clk = 0;
        rst = 0;
        #20 $finish;
    end

    always
        #0.5 clk = ~clk;

    always @(posedge clk)
        $display("count: %d\n", count,
            "c_out: %b\n", c_out);

    dec_counter counter(
        .clk(clk),
        .rst(rst),
        .count(count),
        .c_out(c_out)
    );
endmodule
```

## ssd\_driver\_tb.v

 


Figure 5: The resulting waveform after running our ssd\_driver testbench.

This testbench exercises the ssd\_driver module as it mutliplexes across 4 different seven segment display anodes. It'll print out which anode is active to the screen, along with the corresponding cathodes that should be lit for that particular anode.

```
module ssd_driver_tb;
    reg clk;
    wire [7:0] cathode;
    wire [3:0] anode;

    reg [3:0] i;
    reg [3:0] j;
    reg [3:0] k;
    reg [3:0] l;

    wire [7:0] i_ssd;
    wire [7:0] j_ssd;
    wire [7:0] k_ssd;
    wire [7:0] l_ssd;

    initial begin
        clk = 0;
        i = 0;
        j = 0;
        k = 0;
        l = 0;
        $monitor("At time: %t\n", $time,
            "cathode: %b\n", cathode,
            "anode: %b", anode);
        # 10000 $finish;
    end
end
```



```

always begin
    #5 clk = ~clk;
end

ssd_converter i_converter(
    .n(i),          // input
    .ssd(i_ssd)     // output
);

ssd_converter j_converter(
    .n(i),          // input
    .ssd(j_ssd)     // output
);

ssd_converter k_converter(
    .n(i),          // input
    .ssd(k_ssd)     // output
);

ssd_converter l_converter(
    .n(i),          // input
    .ssd(l_ssd)     // output
);

ssd_driver driver(
    .clk(clk),
    .digit1(i_ssd),
    .digit2(j_ssd),
    .digit3(k_ssd),
    .digit4(l_ssd),
    .cathode(cathode),
    .anode(anode)
);

endmodule

```

## Conclusion

We broke our stopwatch down into a series of submodules which helped speed our development and testing process. Testing for this project was rather difficult because any testbenches that contained a clock that went anywhere near as fast as the FPGA's onboard clock would take quite a while – testing with a 200 MHz clock was clearly not an option. This meant that testing had to be done on a per module basis, and that kept our testbenches fairly short and clean.

The features of our design mapped pretty clearly to a specific module that implements it. The fields of our stopwatch display are driven by two counter modules, each of which depends on two `dec_counter` modules, one for each digit (a field is two digits representing either seconds or minutes). These counters are then fed into `ssd_converter` which turns them into seven segment display inputs. These are then passed through a blink module, which is responsible for blinking the fields on and off at 4Hz when in adjust mode. Finally, these digits are multiplexed by a single `ssd_driver` module which displays all four digits by quickly rotating the anode that is connected.

Inputs to our FPGA, specifically button inputs, are debounced using the debouncer module. This module will track the history of the button input, looking for some length of a steady “high” state followed by a “low” state, and will synchronize the button output on a rising clock edge.

This project was difficult because there were so many different parts, in particular, we had a lot of trouble with the counter module. This module often reset too early or not at all because we had to hard-reset the seconds counter once it hit 59 seconds. This proved more difficult than we thought because `dec_counters` naturally reset when they hit 9, so we had to check to see whether the tens place was “6” at every clock cycle and ensure that the counter registered the call to reset on the next clock cycle when we found a 6.